

1.OHM'S LAW

Aim: To determine resistivity of a given wire by plotting a graph of potential difference versus current.

Apparatus: A wire of unknown resistance , battery eliminator,screw gauge,voltmeter (0-5 V),ammeter,(0– 5A), Rheostat and connecting wires.

Theory: Ohm's law states that the electric current flowing through a conductor is directly proportional to the potential difference across its ends, provided the physical state of the conductor remains unchanged.

If I be the current flowing through the conductor and V the potential difference across its ends, then according to Ohm's law,

$$V \propto I \text{ and hence}$$

$$V = RI \text{(1)}$$

$$R=V/I \text{(2)}$$

where R is the constant of proportionality and is termed as the electrical resistance of the conductor.

If V is expressed in volts and I in amperes, then R is expressed in ohms.

The resistance R, depends upon the material and dimensions of the conductor.

For a wire of uniform cross-section, the resistance depends on the length l and the area of cross-section A. It also depends on the temperature of the conductor

At a given temperature the resistance,

$$R = \rho \frac{l}{A} \text{(3)}$$

where ρ is the specific resistance or resistivity and is characteristic of the material of wire.

From this equation ,

$$\rho = R \frac{A}{\ell} \dots\dots\dots(4)$$

$$A = \pi r^2$$

r is the radius of the wire.

Procedure:

- Connect various components - battery, resistance wire, voltmeter, ammeter and rheostat as shown in circuit diagram.
- Adjust the rheostat knob slightly so that the ammeter and voltmeter show measurable readings.
- Note down the ammeter and voltmeter readings under I and V column
- R is found using the equation $R = V/I$
- Repeat the experiment for different values of current by adjusting the rheostat and note down their corresponding voltage .
- Repeat the steps 2 to 5 to get few sets of readings and find the average value of R
- Plot V-I Graph. The slope of the graph is found

$$\text{slope} = \Delta V / \Delta I$$

The slope of the graph gives the resistance of the wire.

- By using the equation (4) find the resistivity of the given material of wire.

Result:

- The V-I relationship is established through ohm's law experiment and is verified to be true.
- Resistance of given wire

From calculation = Ω

From Graph = Ω

- The resistivity of the material of given wire=..... Ωm


Precautions:

- The connections should be made neat and tight.
- The voltmeter should be connected in parallel and the ammeter in series with the circuit.
- The voltmeter and ammeter should be of proper ranges and their readings should be noted properly.
- The positive of the ammeter and voltmeter should be connected only to the positive of the battery.
- Low resistance rheostat should be used.

Sources of error:

- Instruments may have loose terminals.
- Rheostat may be of high resistance.
- Personal error while noting down the voltmeter and ammeter readings.

Circuit diagram:

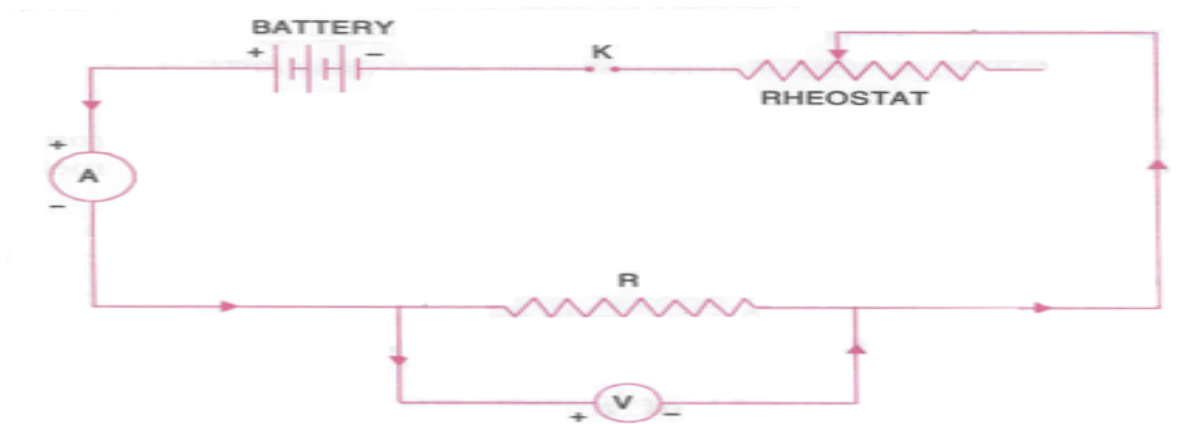


Observation:

Least Count of ammeter=.....A

Least Count of Voltmeter=.....V

No	Ammeter Reading(I) (A)	Voltmeter Reading(V) (V)	Resistance($R=V/I$) (Ω)
1			$R_1=$
2			$R_2=$
3			$R_3=$
4			$R_4=$
5			$R_5=$
6			$R_6=$
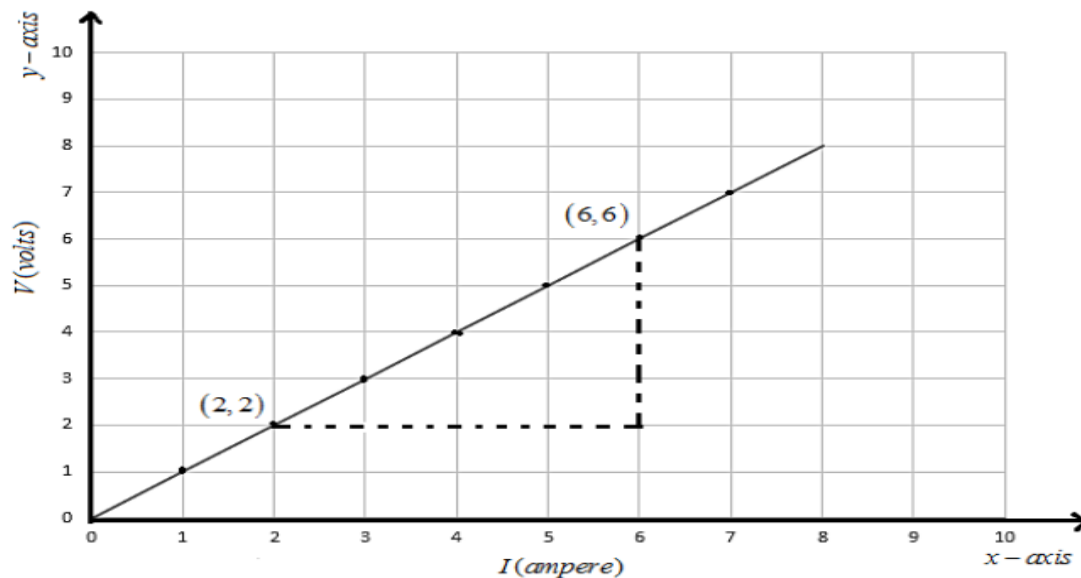
$$\text{Mean Resistance (R)} = \frac{R_1+R_2+R_3+R_4+R_5+R_6}{6} = \dots\dots\dots\Omega$$



(You have to draw the graph on the graph paper with values you got.)

Slope of the Graph, $R = \Delta V / \Delta I = \dots\dots\dots \Omega$

Calculation

Length of the wire, $L = \dots\dots\dots \text{cm} = \dots\dots\dots \text{m}$

Diameter of the wire, $D = \dots\dots\dots \text{mm} = \dots\dots\dots \text{m}$

Resistance (from Graph), $R = \dots\dots\dots \Omega$

Resistivity, $\rho = \frac{R \pi D^2}{4L} = \dots\dots\dots = \dots\dots\dots \Omega \text{m}$